

Ex) Sequential logic implementation using SRFF

Excitation table for SRFF.

$Q(t)$	$Q(t+1)$	$S(t)$	$R(t)$
0	0	0	X (Reset or hold)
0	1	1	0
1	0	0	1
1	1	X	0 (Set or hold)

X - don't care

Implement following Mealy state machine using SRFF's.

Present state		Next state	Output		
Input $X(t)$	state $A(t)$	state $A(t+1)$	$f(t)$	$S(t)$	$R(t)$
0	0	0	1	0	X
0	1	0	0	0	1
1	0	1	1	1	0
1	1	1	0	X	0

These two columns are added for SRFF implementation.

Three K-maps are needed for  $f(t)$ ,  $S(t)$  &  $R(t)$ .

$f(t)$   $A(t)$

$X(t)$	0	1
0	1	0
1	1	0

$f(t) = \bar{A}(t)$

$S(t)$   $A(t)$

$X(t)$	0	1
0	0	0
1	1	X

$S(t) = X(t)$


$R(t)$   $A(t)$

$X(t)$	0	1
0	X	1
1	0	0

$R(t) = \bar{X}(t)$


Boolean  
exps  
in mSOP!

Logic diagram

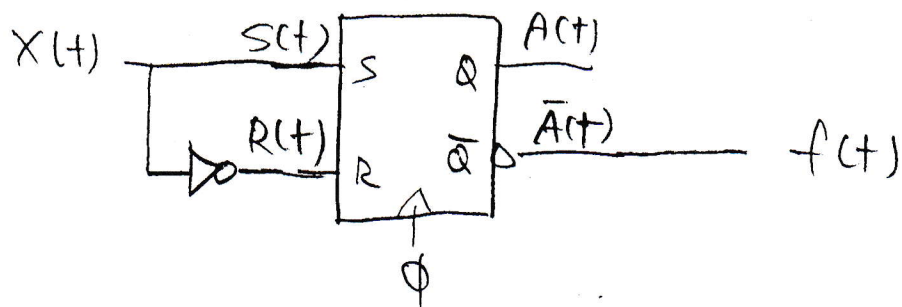

Ex) Implement same state machine w JKFF.

Excitation table

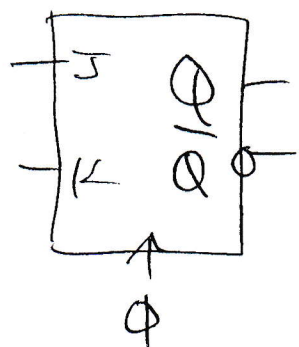

$Q(t)$	$Q(t+1)$	$J(t) \ K(t)$	
0	0	0	X (reset or hold)
0	1	1	X (set or flip)
1	0	X	1 (reset or flip)
1	1	X	0 (set or hold)

$X(t)$	$A(t)$	$A(t+1)$	$f(t)$
0	0	0	1
0	1	0	0
1	0	1	1
1	1	1	0

$J(t)$	$K(t)$
0	X
X	1
1	X
X	0

added for JKFF implementation

$$f(t) = \bar{A}(t)$$

$J(t)$

$X(t)$	$A(t)$	$J(t)$
0	0	0
0	1	X
1	0	1
1	1	X

$$J(t) = X(t) + A(t)$$

$X(t)$

$A(t)$	$X(t)$
0	0
1	X
0	1
1	X

$K(t)$

$X(t)$	$A(t)$	$K(t)$
0	0	X
0	1	X
1	0	0
1	1	0

$$K(t) = \bar{X}(t) + \bar{A}(t)$$



$$J(t) = X(t)$$

$X(t)$

$A(t)$	$X(t)$
0	X
1	1
0	X
1	0

$$K(t) = \bar{X}(t)$$


Logic diagram

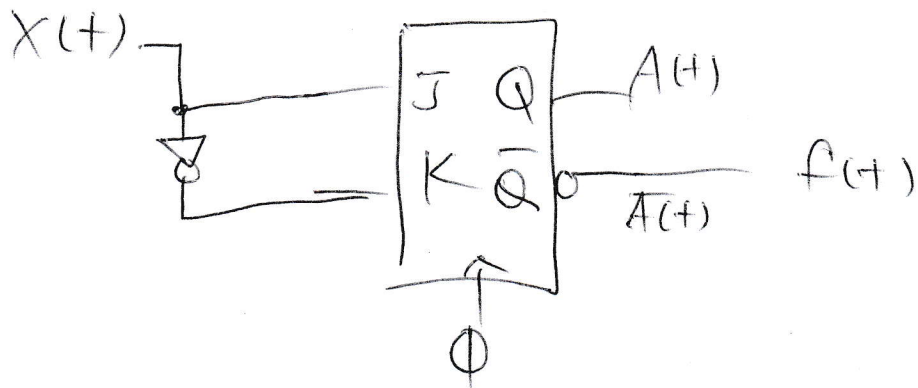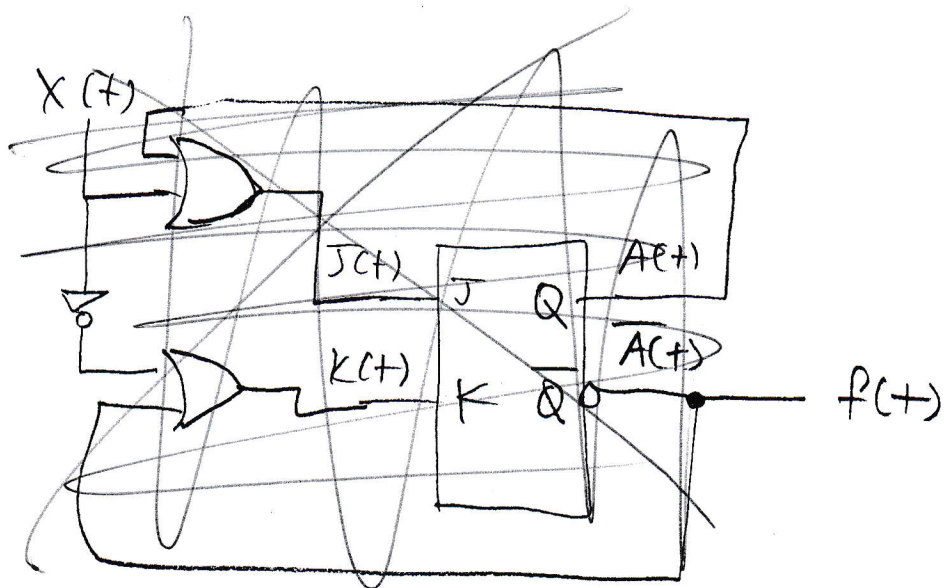

Ex) T FF implementation of the same state machine.

$Q(t)$	$Q(t+1)$	$T(t)$
0	0	0
0	1	1
1	0	1
1	1	0

Excitation table.

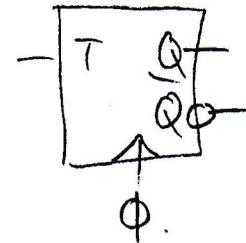

$X(t)$	$A(t)$	$A(t+1)$	$f(t)$	$T(t)$
0	0	0	1	0
0	1	0	0	1
1	0	1	1	1
1	1	1	0	0

$T(t)$   
 $A(t)$   
 $X(t)$

	0	1
0	0	1
1	1	0

$$T(t) = \bar{X}(t) \cdot A(t) + X(t) \cdot \bar{A}(t)$$

manual reduction

Logic diagram

$$= X(t) \oplus A(t)$$

