

CpE2210

Introduction to Digital Logic

Dr. Minsu Choi
CH 5: Digital Hardware & Logic Components



MISSOURI UNIVERSITY OF SCIENCE AND TECHNOLOGY

Hardware?


- The physical realization of a digital element or system.
- How to represent logic 0 and logic 1 states?
 1. Voltage V , which has units of volts (v).
 2. Electrical current I , which has units of ampres (A or amps).
- Two are related: a voltage causes electrical current to flow.
- Most digital logic chips use two different voltage ranges to define logic 0 and logic 1 conditions.



MISSOURI UNIVERSITY OF SCIENCE AND TECHNOLOGY

Power Supply

 
- All electronic networks require a power supply to operate.
- In digital circuits, the power supply is usually modeled as a voltage source with a value that we will denote by V_{DD} (usually 5v, 3.3v or 2.5v).
- Ex) schematic diagram of a digital system with a power supply (since the drawing shows the "scheme" used to construct the circuit).



positive side voltage is higher as much as V_{DD} volts.


Logic Levels

 - Logic 0 \rightarrow 0v and Logic 1 \rightarrow V_{DD} (ex., 5v), in general.
 - Low voltage represents logic 0 & high voltage represents 1 \rightarrow called positive logic.
 - High voltage represents logic 0 & low voltage represents 1 \rightarrow called negative logic.
- Two voltage ranges are used in practice.




Digital Integrated Circuits

 - ICs (Integrated Circuits) = Computer chips.
- Dual inline package (DIP) is very common packaging technology for computer chips.



 - To build more complex digital systems -> use PCB (Printed Circuit Board).




Silicon chip inside

=> complex circuit is fabricated on a Silicon chip by optical lithography.

Pin-Out Diagram

 
- The logic functions that a particular chip implements are usually shown by embedding equivalent logic diagrams in package outline drawings.
- Ex) Quad-AND chip. V_{CC} is an alternative notation for the power supply voltage. $\approx V_{DD}$.



ex) $pm3 = pm1 \cdot pm2$.

Different Packaging Technologies?

 - PGA (Pin Grid Array)
is used for most microprocessor chips, since larger chip can be embedded and larger # of pins can be allocated.
- There are different variations – INTEL's LGA775 and AMD's Socket939.



ICs can be categorized with respect to the # of gates inside

IC Integration Levels


- SSI (Small-Scale Integration): ICs with a few gates.
- MSI (Medium-Scale Integration): ICs with a few hundred gates.
- LSI (Large-Scale Integration): 1K – 100K gates.
- VLSI (Very Large-Scale Integration): a few million gates.
- ULSI (Ultra Large-Scale Integration): around one billion gates.
- Ex) INTEL ~~Pentium 4~~ ^{SIX core i7} processor has about ~~125~~ million gates.

1.27 billion

Logic Delay Times

- Waveform (a plot of a variable as a function of time) is used to measure the behavior of a gate.


- Ex)

 

(a) Logic gate



→ input waveform

 

→ output waveform


(b) Ideal waveforms

- In the real world, a voltage cannot change instantaneously.


⇒ There should be some delays for $0 \rightarrow 1$ & $1 \rightarrow 0$ transitions

Output Switching Times

 - Two time intervals must be considered:
 - t_{LH} , the output low-to-high time, also called the rise time, t_r .
 - t_{HL} , the output high-to-low time, also called the fall time, t_f .
 - By convention, these time intervals are not measured between 0v to V_{DD} , but represent the transition required between 10% to 90% voltage levels, as shown below.



(a) Logic gate

 

(b) Low-to-high and high-to-low times

Continued,

- The minimum amount of time needed for the gate to switch from 0 to 1 then back again is given by:

$$t_{min} = t_{LH} + t_{HL}$$

- The maximum switching frequency is:

$$f_{max} = \frac{1}{(t_{LH} + t_{HL})} \text{ [in Hz]}$$

- =max # of logic transitions that the gate can make in 1 sec.

- Ex) $t_{LH} = 7.2 \text{ ns}$ & $t_{HL} = 3.9 \text{ ns}$, $f_{max}?$


$$f_{max} = \frac{1}{7.2 \times 10^{-9} + 3.9 \times 10^{-9}} = 90.09 \text{ MHz}$$

(≈ 90.09 million transitions per sec max)

Propagation Delay

- It can be hard to keep track of both delay times for every logic gate.
- At the logic design level, it is simpler to introduce a single delay time that represents an average switching time, called “propagation delay”, from the input to the output.
- This is to include the physical delay of a logic signal as it “propagates” through a chain of gates.

Inverter Gate Example

 

- Then, t_p (=propagation delay) = $1/2 (t_{PHL} + t_{PLH})$
or $=\max(t_{PHL}, t_{PLH})$, alternatively.

Fan-In & Fan-Out

- The fan-in of a digital logic gate refers to the number of inputs.
- Ex) inverter has fan-in of 1 and NAND2 has fan-in of 2.
- The fan-in provides information about intrinsic speed of the gate -> the propagation delay increases with the fan-in.
- Ex) OR2 is faster than OR3.

Continued,

- The switching time of an electronic gate depends on the number of gates that are driven (or connected) at the output.
- The fan-out of a gate is the number of gates that are driven by the output, and it depends how the gate is used in the logic chain -> increasing the fan-out slows down the logic flow through the gate.
- If no additional gate -> no load (fan-out=0)

ex) $A \xrightarrow{t_{p0}} \neg A$ no load propagation delay.

- Fan-out=1 ->

$\neg A \xrightarrow{t_{p1}} \neg \neg A$
 $t_{p1} = t_{p0} + 1 \cdot t_{PL}$ additional delay time needed to drive the load (next inverter).

- Fan-out=N ->

$\neg A \xrightarrow{t_{pN}} \neg \neg \neg A$ N gates

$$t_{pN} = t_{p0} + N \cdot t_{PL}$$

Logic Cascades and Delays

- Ex) linear chain of 4 inverters.

$A(t) \xrightarrow{t_{d1}} \neg A \xrightarrow{t_{d2}} \neg \neg A \xrightarrow{t_{d3}} \neg \neg \neg A \xrightarrow{t_{d4}} \neg \neg \neg \neg A = B(t)$

$$t_d = t_{d1} + t_{d2} + t_{d3} + t_{d4}$$


Fan-in & fan-out delays must be considered.

$$t_{d4} = \underbrace{t_{to, NOT}}_{\text{no-load P.D.}} + \underbrace{t_L}_{\text{The load at the forth gate is not specified. So, } t_L \text{ is used.}}$$

$$t_d = \underbrace{4 \cdot t_{to, NOT}}_{\text{no-load prop delay}} + \underbrace{3 t_{PL, NOT}}_{\text{fan-out delay}} + t_L$$

Continued,

 - Ex) Inverter chain with increased internal delay.



$$t'_a = \underbrace{4 \cdot t_{PD,NOT}}_{\substack{\text{no-load} \\ \text{prop delay}}} + \underbrace{6 \cdot t_{PL,NOT}}_{\substack{\text{6 fan-outs} \\ \text{driven}}} + t_L$$


⇒ takes more time because of more fan outs!

Application to Digital Circuits


- Transitions 0->1 and 1->0 take time.
- The switching time of every digital electronic network is governed by any resistance and capacitance in the network.
- Parasitic elements: unwanted resistance and capacitance contributions that cannot be eliminated and that act to slow down the network response.
- So, keeping R and C as small as possible is desired!

Transmission Lines

 - Another type of logic delay arises when we analyze the physics of transmitting a voltage along a wire.



 - Transmission line signal delay ($= t_s$) + the voltage at the end of transmission line takes time to "build up" to the final value $= t_d$.




Digital Logic Component Concept

- It is very difficult to keep track of each gate in designing a large digital system such as a computer.
- The hierarchical design approach where a large ("macro") function is defined using a large block is called a digital component (= element, unit or module).
- Ex)

$$f = f_0(a,b,c,d) \text{ if } s_1, s_0 = 00$$

"	1	"	01
"	2	"	10
"	3	"	11


Control s_1, s_0

 

Control bits select internal functions.

⊛ XNOR is the equivalence function.

Block-diagram

 

4-Bit Equality Detector


- Suppose that we have two 4-bit words

$$a = a_3 a_2 a_1 a_0 \quad b = b_3 b_2 b_1 b_0$$

- That we wish to compare.

if $(a=b)$ then $f=1$ else $f=0$

 
$$\text{So, } f = (a_3 \oplus b_3) \cdot (a_2 \oplus b_2) \cdots (a_0 \oplus b_0)$$




internal circuitry.

BCD Validity Detector

 - Bit patterns from 0000 to 1001 are used.
- How can we design a detector?
- If (ABCD is valid) then $F=0$ else $F=1$.
- Let's build a K-map!




$$F = AB + AC = A(B + C)$$

 

BCD Validation Unit.

⊛ D is "don't care"

Select S_1, S_0

 

F.T.

S_1, S_0	D_3	D_2	D_1	D_0
00	0	0	0	1
01	0	0	1	0
10	0	1	0	0
11	1	0	0	0

Line Decoders


- Line decoder is a circuit that allows us to "activate" an output line by specifying a control word.
- Ex) Active-high 2/4 decoder

$$D_0 = \overline{S_1} \cdot \overline{S_0}$$

$$D_1 = \overline{S_1} \cdot S_0 \Rightarrow$$

$$D_2 = S_1 \cdot \overline{S_0}$$


$$D_3 = S_1 \cdot S_0$$

 

> 2-bit binary word selects the output port to be activated \Rightarrow called Active-high decoder.

\Leftarrow internal circuitry for the 2/4 decoder.

S_1, S_0 select

 

output

Active-Low 2/4 Decoder

$$D_0 = \overline{\overline{S_1} \cdot \overline{S_0}}$$

$$D_1 = \overline{\overline{S_1} \cdot S_0}$$

$$D_2 = \overline{S_1 \cdot \overline{S_0}}$$

$$D_3 = \overline{S_1 \cdot S_0}$$

\Rightarrow replace AND gates of active-high decoder to NAND gates.

or, by DeMorgan's rule...

$$D_0 = S_1 + S_0$$

$$D_1 = S_1 + \overline{S_0}$$

$$D_2 = \overline{S_1} + S_0$$

$$D_3 = \overline{S_1} + \overline{S_0}$$


\Rightarrow NOT & OR gates can be used.

\Rightarrow Either way, the external behavior remains the same regardless of the internal circuit details.

Multiplexer (MUX)

- A MUX is a logic component that has several inputs but only a single output. It provides the capability to direct one of the inputs to the outputs.

- Ex) 4:1 MUX

 


S_1	S_0	F
0	0	P_0
0	1	P_1
1	0	P_2
1	1	P_3


Sop form

$$F = \bar{S}_1 \bar{S}_0 \cdot P_0 + \bar{S}_1 S_0 \cdot P_1 + S_1 \bar{S}_0 \cdot P_2 + S_1 S_0 \cdot P_3$$

 4:1 MUX: Internal Circuitry and IEEE Symbol



IEEE symbol

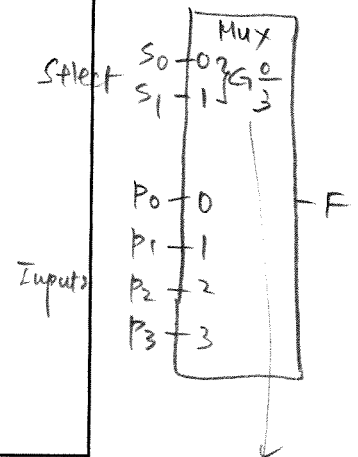


G-dependance notation

(select bits S_1 & S_0)

select output 4

signal $P_0 \sim P_3$

8:1 MUX

 

- Internal circuitry will be very complex.
- 2 4:1 MUXs & 1 2:1 MUX can be combined to implement 8:1 MUX.
- -> Hierarchical design approach.

Continued,

- The select word $s_2s_1s_0$ can be split into two groups: s_1s_0 to control the 4:1 MUXs and s_2 to select a desired output from them.
- Two internal signal x_1 and x_2 can be defined as:


$$x_1 = \bar{s}_1\bar{s}_0p_0 + \bar{s}_1s_0p_1 + s_1\bar{s}_0p_2 + s_1s_0p_3$$

$$x_2 = \quad \quad p_4 \quad \quad p_5 \quad \quad p_6 \quad \quad p_7$$

- Then,

$$f = \bar{s}_2 \cdot x_1 + s_2 \cdot x_2$$

Completed 8:1 MUX Design

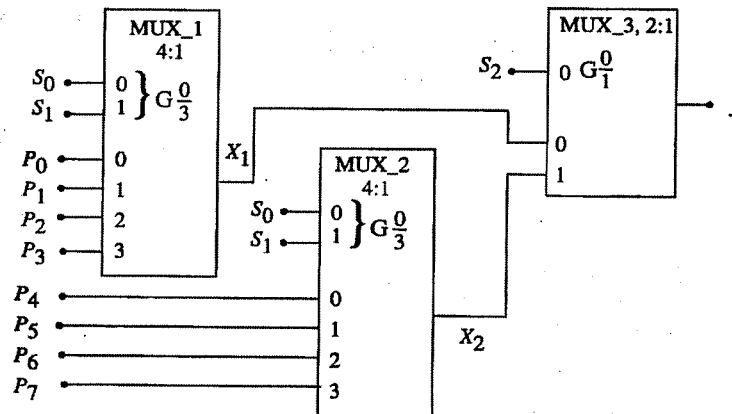

MUXs as Logic Elements

- A MUX can be programmed to function as a logic element.
- Ex) 4:1 MUX OR implementation.

The output equation of 4:1 MUX is...

$$f(x, y) = \bar{x}\bar{y}P_0 + \bar{x}yP_1 + x\bar{y}P_2 + xyP_3$$

T.T of OR is

xy	f
00	0
01	1
10	1
11	1

replace


$$\begin{aligned} P_0 &= 0 \\ P_1 &= 1 \\ P_2 &= 1 \\ P_3 &= 1 \end{aligned}$$

$$f = \bar{x}\bar{y} + x\bar{y} + xy$$

↓ K-map reduction

$$f = x + y$$

xy	0	1
0	0	1
1	1	1

 


⊗ Input vars → control bits of MUX

Continued,


■ Ex) XOR

x	y	f
0	0	0
0	1	1
1	0	1
1	1	0

 

■ Ex) XNOR

x	y	f
0	0	1
0	1	0
1	0	0
1	1	1

 


VHDL Description of 4:1 MUX

```
entity mux4 is
  port(d0, d1, d2, d3: in
        bit; s : in bit_vector(1
        downto 0); f : out bit);
end mux4;
```


```
architecture basic of
  mux4 is
```
 
```
begin
  f<=d0 when (s="00")
  else
  f<=d1 when (s="01")
  else
  f<=d2 when (s="10")
  else
  f<=d3 when (s="11")
end basic;
```



Demultiplexer (DEMUX)

 - A DEMUX is the opposite of a MUX. It takes a single input and directs it to one of several outputs.
- Ex) ~~1:4~~ DEMUX



VHDL Code

```

entity demux1_4 is
    port(x, s: in bit;
          p0,p1,p2,p3 : out bit);
end demux1_4;


architecture operation of
    demux1_4 is
        begin
            if s="00" then
                p0<=x;
                p1<='0';
                p2<='0';
                p3<='0';
            else if s="01" then
                ...
            end operation;
        end operation;
    end architecture;
  
```

Binary Adders

- Arithmetic functions such as addition and subtraction can be performed using binary numbers. These types of operations are central to building a computer.
- 4 cases can be identified for 1-bit addition:
 - $0 + 0 = 0$
 - $0 + 1 = 1$
 - $1 + 0 = 1$
 - $1 + 1 = 0$ with a carry of 1 (called "carry bit")
- The output column is equivalent to XOR function.




\Rightarrow XOR

 

Full Adder

- A logic network that provides the operations needed to add the bits in an arbitrary column.
- 3 input bits: a_n , b_n (data bits) and c_n (carry-in bit from the column immediately to the right).
- 2 output bits: s_n (sum bit) and c_{n+1} (carry-out bit).

Block Diagram and Truth Table

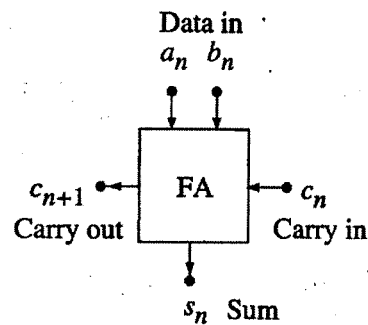

(a) Block diagram

a_n	b_n	c_n	s_n	c_{n+1}
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

(b) Function table

Simplified Function Forms of s_n and c_{n+1}


\Rightarrow K-maps problem not to be effective.

$$\begin{aligned}
 S_n &= \bar{a}_n \bar{b}_n \bar{c}_n + a_n \bar{b}_n \bar{c}_n + \bar{a}_n b_n \bar{c}_n + a_n b_n \bar{c}_n \\
 &= (\bar{a}_n \bar{b}_n + a_n \bar{b}_n) \bar{c}_n + (\bar{a}_n b_n + a_n b_n) \bar{c}_n \\
 &= (a_n \oplus b_n) \bar{c}_n + (\overline{a_n \oplus b_n}) c_n \\
 &= \boxed{a_n \oplus b_n \oplus c_n} \quad \Leftarrow \text{Odd function.}
 \end{aligned}$$


$$\begin{aligned}
 C_{n+1} &= a_n b_n \bar{c}_n + \bar{a}_n b_n c_n + a_n \bar{b}_n c_n + a_n b_n c_n \\
 &= a_n b_n (\bar{c}_n + c_n) + c_n (\bar{a}_n b_n + a_n b_n) \\
 &= \boxed{a_n b_n + c_n (a_n \oplus b_n)}
 \end{aligned}$$

Half Adder

 - A special case of the full adder when $c_n=0$ (no carry-in bit considered).



 $S_n, S_n = a_n \oplus b_n, C_{n+1} = a_n \cdot b_n$




Parallel Adders

- Half-adders and full-adders are used to add individual bits together. An extension of this problem is the addition of two n -bit binary words.

- Ex) $A = a_3 a_2 a_1 a_0$ & $B = b_3 b_2 b_1 b_0 \Rightarrow 4\text{-bit adder}$
Let's break down the problem explicitly by writing the addition procedure out as:

 - This shows that we can use a single-bit adder for each column and connect the carry-out bit to the adjacent column to the right.



Overflow Bit

- Also note that the sum may be larger than 4 bits.
- So, an overflow bit c_o is provided such that $c_o = 0$ means that 4 bits are sufficient to express the sum, while $c_o = 1$ implies that the sum requires more than 4 bits.

■ Ex)

$$\begin{array}{r}
 0101 \\
 + 0111 \\
 \hline
 1100
 \end{array}$$

no overflow


$$\begin{array}{r}
 1110 \\
 + 1110 \\
 \hline
 11100
 \end{array}$$

overflow

⇒ now the result requires 5 bits (overflow). This is because the answer (27_{10}) is larger than the max value (15_{10}) that can be represented by 4-bit word!


Parallel Adder Design with Ripple Carry Scheme

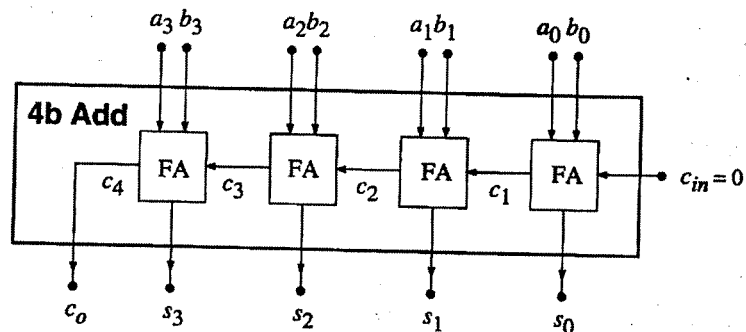- The carry "ripples" from the right to the left.




Timing

 - There are two cases we must consider:
 - FA generates s first, then c .
 - FA generates c first, then s .




(a) FA produces sum bit first

 

 (b) FA produces carry-out bit first


8-Bit Adder Design using Cascaded 4-Bit Adders



- Likewise, 16-bit or more can be designed.

IEEE Adder Symbol

ex) 4-bit adder

 

- P: input word 1
- Q: input word 2
- Sigma: output word
- CI: carry-in bit
- CO: carry-out bit

Subtraction

- It is more complex since we need to "borrow".

■ Ex)

$$0 - 0 = 0$$

$$1 - 0 = 1$$

$$1 - 1 = 0$$

$$10 - 1 = 1$$

(using a borrow of 1 from the left)

ex)

$$\begin{array}{r} \overset{\text{"borrow"}}{\curvearrowright} 10 \\ - 01 \\ \hline 01 \end{array}$$

✓

- Very hard to implement with digital network.

More Efficient Way?

- $X - Y = D$ is equivalent to saying that $X + (-Y) = D$ where $Y + (-Y) = 0$.
- So, we can find $(-Y)$. Then, using the adder, add X & $(-Y)$ to perform subtraction.

■ Ex) $Y = Y_3 Y_2 Y_1 Y_0$ $(-Y) = W_3 W_2 W_1 W_0$

then $Y + (-Y) = 0 \Rightarrow$

$$\begin{array}{r} Y_3 Y_2 Y_1 Y_0 \\ + W_3 W_2 W_1 W_0 \\ \hline 0 \ 0 \ 0 \ 0 \end{array}$$

If we choose $W_n = \bar{Y}_n$, then the sum in every column is automatically $(1+0)=1$, so that:

$$\begin{array}{r} Y_3 Y_2 Y_1 Y_0 \\ + \bar{Y}_3 \bar{Y}_2 \bar{Y}_1 \bar{Y}_0 \\ \hline 1 \ 1 \ 1 \ 1 \end{array} \leftarrow \text{should be } \phi \phi \phi \phi$$

Idea!! add 1 to make it $\phi \phi \phi \phi$.

1111
+1
1 0000
all 0s
⇒ the goal
accomplished
ignore carry.

1's Complement and 2's Complement

- Then, how we can express $(-Y)$ in binary?
- 2's complement number can be used.
 - First, complement each bit: called 1's complement.
 - Then, add 1 to it: called 2's complement.
 - $Y + 2$'s complement $Y = 0$, if we discard overflow bit.
 - So, $(X - Y) = X + 2$'s complement $Y \rightarrow$ we can use the adder to perform subtraction.

■ Ex) $X = 0101$ and $Y = 0011$. Then, $(X - Y) = ?$

① 1's complement $(Y) = 1100$

② 2's " $(Y) = 1100 + 1 = 1101$

③ add them up.

$$\begin{array}{r} 0101 \\ + 1101 \\ \hline \end{array}$$


discard \leftarrow 1 0010 \rightarrow result.

\Leftarrow


$$\begin{aligned} X &= 5_{10} \\ Y &= 3_{10} \\ X - Y &= 2_{10} \end{aligned}$$

Subtraction Logic Circuit

 - XOR gate can be used to generate 1's complement number.
- C_{in} must be 1 so that we add 1 to 1's complement to make 2's complement.



SUB	b_n	$f = SUB \oplus b_n$
0	0	0
0	1	1
1	0	1
1	1	0

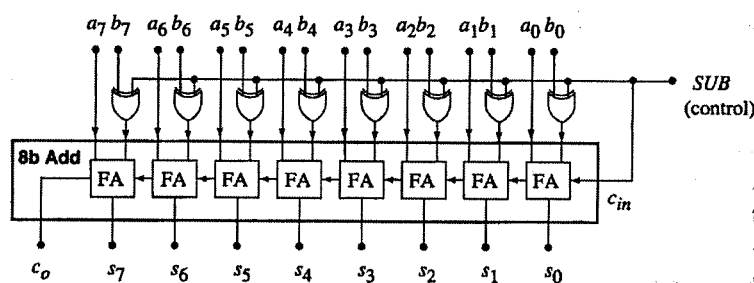

Positive and Negative Integers in 2's Complement

- n-bit binary word has 2^n bit patterns.
- The total number of bit patterns is divided into two groups.
- If MSB is 0, positive integer.
- If MSB is 1, negative integer.
- So MSB is also called as "sign bit".
- Since all-zero bit pattern is used to represent 0, the range of positive values is one less than the range of negative values.
- For example, 8-bit 2's complement word has 256 bit patterns. So, it is possible to express -128_{10} to $+127_{10}$.

S	a ₆	a ₅	a ₄	a ₃	a ₂	a ₁	a ₀
-128	64	32	16	8	4	2	1

8-Bit 2's Complement Number

- The MSB is used as sign bit of -2^7 weight and the other bits have weight of 2^i .

$$A = \boxed{S} \ a_6 \ a_5 \ a_4 \ a_3 \ a_2 \ a_1 \ a_0$$


Sign bit of -2^7 weight = $S \times (-2^7)$ positive bin #

- Ex) $0000 \ 0001 = 1_{10}$
 $1000 \ 0001 = -128_{10} + 1_{10} = -127_{10}$
 \vdots
 $1111 \ 1111 = -128_{10} + (64_{10} + 32_{10} + \dots + 1_{10}) = -1_{10}$

Multiplication

- AND function can be used to implement 1-bit multiplication.
 
$$\begin{array}{l} 0 \times 0 = 0 \\ 0 \times 1 = 0 \\ 1 \times 0 = 0 \\ 1 \times 1 = 1 \end{array} \Rightarrow \text{AND function}$$



- For multi-bit multiplication, 1-bit multiplier and HA can be used.

- Ex) 2-bit multiplication


$$\begin{array}{r} a_1 \ a_0 \\ b_1 \ b_0 \\ \hline a_1 b_0 \ a_0 b_0 \\ a_1 b_1 \ a_0 b_1 \\ \hline \end{array}$$

Product $\Rightarrow P_3 \ P_2 \ P_1 \ P_0$

ex)


$$\begin{array}{r} 11 \\ \times 10 \\ \hline 00 \\ 11 \\ \hline \boxed{110} \end{array}$$

2-Bit Multiplier Internal Circuitry

 


Transmission Logic Gate

 
- TGs are logic-controlled switches that can be used to construct a wide variety of logic networks.
- CMOS TG has very simple structure:




(a) Transmission gate

 

(b) Open switch

 


(c) Closed switch

 

If $S=0$, then open. (B is not determined by A)
 If $S=1$, then closed ($B=A$)

2:1 MUX using TGs

 


(a) Logic diagram

S	F
0	P_0
1	P_1

(b) Function table


4:1 MUX using TGs

 

TG XOR and XNOR Gates


EX) XOR
 
$$F = A \cdot \bar{B} + \bar{A} \cdot B = A \oplus B$$



EX) XNOR
 
$$F = A \cdot B + \bar{A} \cdot \bar{B} = \overline{A \oplus B}$$



Program Completed

University of Missouri-Rolla

© 2003 Curators of University of Missouri

UMR

UNIVERSITY OF MISSOURI-ROLLA
The Name. The Degree. The Difference.