

CpE2210

Introduction to Digital Logic

Dr. Minsu Choi

CH 4: Combinational Logic Design



MISSOURI UNIVERSITY OF SCIENCE AND TECHNOLOGY

What is Combinational Logic Design?

Combinational logic deals with networks that use logic gates to combine the input variables as needed to produce logic functions -> the value of the output is determined by the current values of the inputs.

Logic diagrams, truth tables (= function tables) and Boolean expressions are used to represent combinational logic designs.



MISSOURI UNIVERSITY OF SCIENCE AND TECHNOLOGY

Canonical Logic Forms

- Two types of structured forms are especially useful in logic design -> Sum-of-Products (SOP) & Product-of-Sums (POS).
- SOP form
- A SOP expression consists of AND terms that are ORed together.
- For a function to be in canonical SOP structure, every variable must appear in each term in either normal or complemented form, otherwise, the function is simply SOP form -> Canonical SOP \neq SOP.

Example

ex) Suppose that we have variables A, B and C

$$f = ABC + \bar{A}BC + A\bar{B}C + AB\bar{C}$$

$$g = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + AB\bar{C}$$

are in canonical SOP form.

$F = AB + \bar{A}C + B\bar{C}$ is in SOP form, but not canonical SOP form!

$$G(a,b,c) = a\bar{b}c + \bar{a}bc + \textcircled{ac}$$

is not in canonical SOP form because of \checkmark .

How to Convert SOP into Canonical SOP?

■ Ex) $h(x, y, z) = xy + yz$ we use $(x + \bar{x} = 1, z + \bar{z} = 1)$

$$\begin{aligned}
 &= x \cdot y \cdot 1 + 1 \cdot y \cdot z = x \cdot y \cdot (z + \bar{z}) + (x + \bar{x}) \cdot y \cdot z \\
 &= xy\bar{z} + xyz + x\bar{y}z + \bar{x}yz \\
 &= \underline{xy\bar{z}} + \underline{x\bar{y}z} + \underline{\bar{x}yz}
 \end{aligned}$$

$\downarrow \quad \quad \downarrow \quad \quad \downarrow$
 Each AND term has all variables.
 \Rightarrow Canonical SOP form!

Continued,

- Product-of-Sum form (POS): A POS express consists of OR terms that are ANDed together.

■ Ex) $f(x, y) = (\bar{x} + y) \cdot (x + \bar{y}) \Rightarrow$ canonical POS.

$g(x, y) = x \cdot (x + \bar{y}) \Rightarrow$ POS.

Extracting Canonical Forms

- Truth table (= function table) -> Boolean expression in canonical SOP.
1. Select rows with output = 1.
 2. Look up the input bits & construct AND terms.
 3. Then OR them to get the canonical SOP form.

Examples

A	B	C	f(A,B,C)		g	
0	0	0	0		1	$\leftarrow \bar{A}\bar{B}\bar{C} = 1$
0	0	1	1	$\leftarrow \bar{A}\bar{B}.C = 1$	1	$\leftarrow \bar{A}\bar{B}C = 1$
0	1	0	1	$\leftarrow \bar{A}B\bar{C} = 1$	0	
0	1	1	0		0	
1	0	0	1	$\leftarrow A\bar{B}\bar{C} = 1$	0	
1	0	1	0		0	
1	1	0	0		0	
1	1	1	1	$\leftarrow A.B.C = 1$	1	$\leftarrow ABC = 1$
					1	$\leftarrow ABC = 1$

$$f = \bar{A}\bar{B}.C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

$$g = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C} + ABC$$

Minterms & Maxterms

- Easy ways to express C SOPs & C POSs, respectively.
- Ex) Three variable case A, B, C
 1. If complemented $\rightarrow 0$, if not complicated $\rightarrow 1$.
 2. Then find binary #.
 3. Convert it into decimal.

$$\begin{aligned}\bar{A}\bar{B}\bar{C} &= m_0 \\ 000 &= 0 \rightarrow m_0 \\ \bar{A}\bar{B}C &= m_1 \\ \bar{A}B\bar{C} &= m_2 \\ \bar{A}BC &= m_3\end{aligned}$$

$$\begin{aligned}AB\bar{C} &= m_4 \\ A\bar{B}C &= m_5 \\ AB\bar{C} &= m_6 \\ ABC &= m_7\end{aligned}$$

Examples

$$f(A,B,C) = \bar{A}\bar{B}\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + ABC$$

$$= m_0 + m_3 + m_4 + m_7$$

Summation of minterms $= \sum m(0,3,4,7)$

Summation sign sigma

This shorthand notation provides a compact way to express SOP functions.

ex) Let's expand the function $g(a,b,c) = \sum m(1,4,5)$

$$= m_1 + m_2 + m_5$$

$$= \bar{a}\bar{b}c + \bar{a}b\bar{c} + a\bar{b}c$$

Continued,

■ Maxterm: $M_i = \overline{m_i}$

■ Ex) 3-variable case

DeMorgan's theorem.

$$M_0 = \overline{m_0} = \overline{\overline{A} \cdot \overline{B} \cdot \overline{C}} = A + B + C$$

$$M_1 = \overline{m_1} = A + B + \overline{C}$$

$$M_7 = \overline{m_7} = \overline{A + B + C} = \overline{A} + \overline{B} + \overline{C}$$

→ (If complemented = 1 in this case.
If not complemented = 0)

■ Ex)

$$g = (A + B + \overline{C}) \cdot (A + \overline{B} + \overline{C}) \cdot (\overline{A} + \overline{B} + \overline{C})$$

$$= M_1 \cdot M_3 \cdot M_7 = \prod M(1, 3, 7)$$

product sum
Pi

SOP <-> POS <-> Truth Table

■ Ex) 3-var case

easy.

$$F = m_1 + m_2 + m_5 + m_6 \rightarrow$$

$$= \sum m(1, 2, 5, 6)$$

SOP

we should look for entries where the minterms are 0.

POS

ABC	F
000	0
001	1
010	1
011	0
100	0
101	0
110	1
111	0

T.T.

$$M_0 = \overline{m_0} \quad M_3 = \overline{m_3} \quad M_4 = \overline{m_4} \quad M_7 = \overline{m_7}$$

$$\text{so, } F = \prod (0, 3, 4, 7)$$

$$M_i = \overline{m_i}$$

↗

- ① Select rows with output = 0 where maxterm = 1 & minterm = 0.
- ② Find maxterm expression.

Exclusive-OR & Equivalence Operation


- When only a single input is 1 exclusively the output is 1.

XOR and XNOR

XOR \rightarrow XOR (read "o-plus")

A B | A \oplus B

0	0	0
0	1	1
1	0	1
1	1	0

 

\Rightarrow SOP

$$A \oplus B = A\bar{B} + \bar{A}B$$

POS?

$$A \oplus B = (A+B) \cdot (\bar{A} + \bar{B})$$


$$XNOR = \overline{A \oplus B} = A\bar{B} + \bar{A}B \text{ in SOP.}$$

$$\Rightarrow A \oplus B = 1 \text{ iff } A \neq B$$

\Rightarrow XNOR is referred to as the equivalence function.



A B | A \odot B

0	0	1
0	1	0
1	0	0
1	1	1

 

"equals to 1"

IEEE Symbols

  

- 3 input and higher circuits \rightarrow cascading.

ex) $A \oplus B \oplus C$ $\begin{cases} = 0 & \text{if there are an even \# of 1s at the input} \\ = 1 & \text{"odd"} \end{cases}$

\rightarrow So called odd-function


A	B	C	A \oplus B \oplus C
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1



=

1	0	1	0
1	1	0	0
1	1	1	1


its even function?

 

$\overline{A \oplus B \oplus C}$ $\begin{cases} = 1 & \text{if there are even \# of 1s} \\ = 0 & \text{"odd \#"} \end{cases}$

Logic Arrays

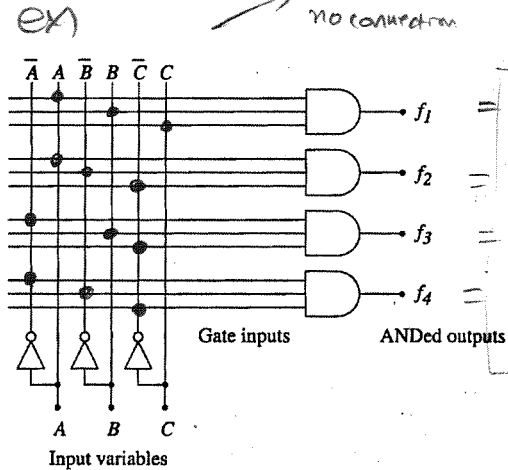- Structured networks that can be configured to produce specific forms of logic expressions.
- AND array (minterms are used to program it)
- Uncommitted AND logic array -> programming (= make connections accordingly)



no connection

Connection.

minterms we want to

phys

$f_1 = m_7 = A \cdot B \cdot C$

$f_2 = m_4 = A \cdot \bar{B} \cdot \bar{C}$

$f_3 = m_2 = \bar{A} \cdot B \cdot \bar{C}$

$f_4 = m_0 = \bar{A} \cdot \bar{B} \cdot \bar{C}$

Continued,

- OR array (produces maxterms)
- Ex)


$$f_1 = X + Y + Z = M_0$$

$$f_2 = \bar{X} + Y + \bar{Z} = M_4$$


$$f_3 = X + \bar{Y} + Z = M_2$$

$$f_4 = \bar{X} + \bar{Y} + \bar{Z} = M_7$$

 - Combine AND & OR array -> SOP & POS arrays.



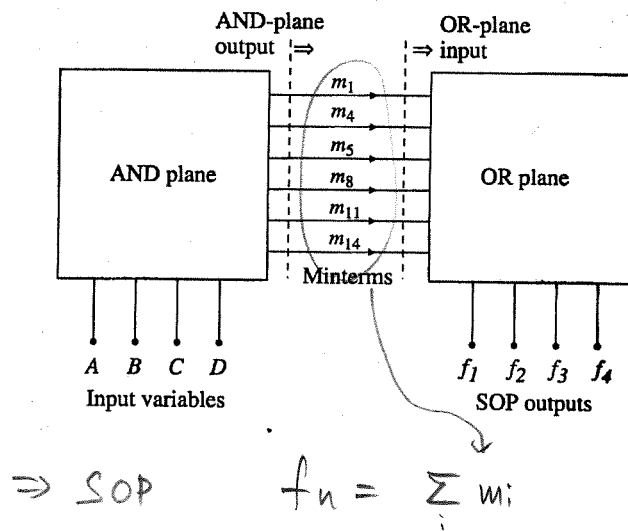AND-OR PLA (Programmable Logic Array) for SOP



OR-AND PLA for POS


 


Figure 3.15 An OR-AND PLA

these are equivalent!
(the second one is simplified version)

Example

 

=> final Boolean functions from the given programmed PLA.

$$h = ABC + \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C}$$

$$g = A\bar{B}C + \bar{A}BC + A\bar{B}\bar{C}$$

$$f = ABC + \bar{A}\bar{B}C + A\bar{B}\bar{C}$$

$$y = \bar{A}\bar{B}C + A\bar{B}C + A\bar{B}\bar{C}$$

Pros and Cons of Logic Arrays

- Pros: Rapid implementation & prototyping of complex digital networks.
- Cons: Resulting circuit will probably not be the most efficient use of gates and the design itself will not be the fastest implementation that can be achieved.
- Complex PLA-based programmable devices are called PLDs (Programmable Logic Devices).
- Good example of PLD: FPGAs (Field-Programmable Gate Arrays) -> very powerful logic circuits that can be used to implement highly complex logic networks.
- CAD tools are used to implement and program custom logic networks on FPGAs.

good example of combinational logic design!

BCD & 7-Segment Display

- Binary-Coded Decimal (BCD) is a binary counting system for the base-10 digits 0 through 9 -> 4 bits required & A, B, C, D denote individual bits.

ABCD	Decimal	ABCD	Decimal
0000	0	0101	5
0001	1	0110	6
0010	2	0111	7
0011	3	1000	8
0100	4	1001	9

⇒ 4 bit binary word to express single dec digit.

- Binary combinations 1010 through 1111 are not used.

Ex) An application of BCD: BCD to 7-segment decoder.


- 7-segment display: a common type of numerical display that usually uses 7 LEDs (Light-Emitting Diodes) to represent decimal digits.

$\begin{array}{c} \text{a} \\ \hline \text{f} | \text{g} | \text{b} \\ \hline \text{e} | \text{c} \\ \hline \text{d} \end{array}$

Formulation of base-10 digits using a 7-seg display

ex) a b c d e f are ON & g is off.

BCD-to-7-Segment Decoder Function

 

- decoder has 7 outputs → 7 functions


- $a = a(A, B, C, D)$
- $b = b(A, B, C, D) \dots$

- SOP expressions?

$$a = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}BC\bar{D} + \bar{A}BCD + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D$$

Find minterms from the column for a then OR them up.

PLA Implementation

 

minterms

m0
m1

m9

Karnaugh Maps (= K-maps)

- Canonical SOP & POS forms can be simplified, but the types of gates and their placement in the logic network will be "random" in that they cannot be predicted -> This design technique is called random logic -> More systematic way? K-maps.
- Karnaugh maps allow us to simplify Boolean functions using a visual mapping technique that helps us recognize Boolean reductions by their locations on a grid.
- The technique of K-maps relies on the following two identities:

$$\begin{array}{l} \uparrow \\ A + \bar{A} = 1 \\ 1 \cdot X = X \end{array}$$

$$\text{ex) } (A + \bar{A}) \cdot X = 1 \cdot X = X$$

- where X is any group of logic variables.

Continued,

- Ex)

$$\begin{aligned} f(A, B, C) &= \underbrace{ABC + AB\bar{C}} + \underbrace{A\bar{B}C + A\bar{B}\bar{C}} \\ &= AB(C + \bar{C}) + A\bar{B}(C + \bar{C}) \\ &= AB + A\bar{B} = A(B + \bar{B}) \end{aligned}$$

↳ has only two gates.

- -> K-maps can do reductions in a systematic way.
 1. Start with a function table.
 2. Map the input-output combinations to a rectangular grid array.
 3. Locate the terms where the identity $(x + \bar{x}) = 1$ can be used to simplify the function.

Continued,

- K-maps can be applied to functions with arbitrary # of variables.
- Only 2, 3, and 4-variable cases will be discussed.
- For more # of variables, computer programs can be used.
(since they are computationally complex).

2-Variable K-maps

- Express the function in grid-like table.
- List all possible minterms & the resulting output value of the function -> $\bar{A}\bar{B}$, $\bar{A}B$, $A\bar{B}$ and AB
- Construct a basic map.

		B	
		0	1
A	0	(m_0) $\bar{A}\bar{B}$	(m_1) $\bar{A}B$
	1	(m_2) $A\bar{B}$	(m_3) AB
- Lookup truth table & construct K-map.
- Locate groups of 1, 2 or 4 adjacent 1s and simplify each group called "one cell".

Examples

EX1 AND

A	B	AB
0	0	0
0	1	0
1	0	0
1	1	1

→ $\begin{array}{c|cc} A \backslash B & 0 & 1 \\ \hline 0 & 0 & 0 \\ 1 & 0 & 1 \end{array}$ Since we have only one, no reduction can take place alone
 $m_3 = AB$ (AND)

EX2 $AB \mid f(A,B)$

A	B	f(A,B)
0	0	1
0	1	1
1	0	1
1	1	0

→ $\begin{array}{c|cc} A \backslash B & 0 & 1 \\ \hline 0 & 1 & 1 \\ 1 & 1 & 0 \end{array}$ $\bar{A}\bar{B} + \bar{A}B = \bar{A}(B+B) = \bar{A}$
 $\bar{A}\bar{B} + AB = \bar{B}(\bar{A}+A) = \bar{B}$

So, $f = \bar{A} + \bar{B} = \overline{A \cdot B}$ (NAND)

De Morgan's theorem.

EX3

A	B	f	g
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	0

A \ B	0	1
0	0	1
1	1	0

→ $f = A + B$ (OR)

A \ B	0	1
0	1	0
1	0	0

De Morgan's theorem.

$g = \bar{A}\bar{B} = \overline{A+B}$ (NOR)

3-Variable K-Maps

- Create a map using the variable A with B,C (or A,B with C) so that adjacent boxes differ by only one bit entry.

ex)

BC	00	01	11	10
A=0	$\bar{A}\bar{B}\bar{C}$	$\bar{A}\bar{B}C$	$\bar{A}BC$	$\bar{A}B\bar{C}$
A=1	$A\bar{B}\bar{C}$	$A\bar{B}C$	ABC	$AB\bar{C}$

BC	00	01	11	10
0	m_0	m_1	m_3	m_2
1	m_4	m_5	m_7	m_6

- 1, 2, 4 or 8 adjacent 1s can be grouped and reduced.
- Left and right edges are also adjacent; allowing us to "wrap" the map into a cylinder.

Examples

ex) BC 00 01 11 10

A				
0	0	0	1	1
1	1	0	1	0

$$A\bar{B}\bar{C} \quad (A+\bar{A})BC = BC$$

$$\bar{A}B(C+\bar{C}) = \bar{A}B$$

$$f = A\bar{B}\bar{C} + BC + \bar{A}B$$

$$= A\bar{B}\bar{C} + B(\bar{A} + C)$$

→ further algebraic reduction, if possible.

ex) BC 00 01 11 10

A				
0	1	0	0	1
1	1	1	1	0

$$(A+\bar{A}) \cdot (B+\bar{B})\bar{C} = \bar{C}$$

$$A \cdot (C+B+\bar{B}) \cdot C(C+\bar{C}) = A$$

$$g = A + \bar{C}$$

Summary of Simplification Rules

- A group of one minterm gives a term with all three factors A, B and C.
- A group of two minterms reduces to a term with two factors.
- A group of four minterms reduces to a term with one factor.
- A group of all eight minterms is equivalent to a logic 1.


1s should be grouped in order that reduction rule $(A+\bar{A}) \cdot C = C$ can be used.

of groups should be minimized (\leq 1s in each group should be maximized)

"Don't Care" Conditions


- The output produced by a particular set of inputs can be either 0 or 1 without affecting the behavior of the function -> called "don't care" condition & denoted by X.

■ Ex)

 

$$f = A \cdot B + \bar{C}$$


If considered as 0's

 

$$f = A \cdot B \cdot C + \bar{B} \cdot \bar{C}$$

Alternative 3-Variable Layout

Group A & B rather than B & C.

 

← Top & bottom edges are adjacent in this case.

$$\bar{A} \cdot B \cdot (C + \bar{C}) = \bar{A} \cdot B$$

$$(A + \bar{A}) \cdot \bar{B} \cdot \bar{C} = \bar{B} \cdot \bar{C}$$

$$f = \bar{A} \cdot B + \bar{B} \cdot \bar{C}$$



Don't care minterm notation: $\sum x m(2, 6)$

"Maxterm" : $\prod X M(2, 6)$

4-Variable K-Maps

- Group A,B and C,D to draw a K-map.
- Group 1, 2, 4, 8 or 16 adjacent entries of 1s.
- Top-down and left-right edges are adjacent.

		CD			
		00	01	11	10
AB	00	m ₀	m ₁	m ₃	m ₂
	01	m ₄	m ₅	m ₇	m ₆
	11	m ₁₂	m ₁₃	m ₁₅	m ₁₄
	10	m ₈	m ₉	m ₁₁	m ₁₀

Examples

		CD			
		00	01	11	10
AB	00	1			1
	01		1		
	11				
	10	1	1	1	1

$$(A+\bar{A})\bar{B}(C+\bar{C})\bar{D} = \bar{B}\bar{D}$$

$$(A+\bar{A})B\bar{C}D = B\bar{C}D$$

$$A\bar{B}C(D+\bar{D}) = A\bar{B}C$$

$$f = B\bar{C}D + A\bar{B}C + \bar{B}\bar{D}$$

$$= B\bar{C}D + \bar{B}(AC + \bar{D})$$

		CD			
		00	01	11	10
AB	00	1	1	1	1
	01				
	11				
	10	1	1	1	1

$$(A+\bar{A})\bar{B}(C+\bar{C})(D+\bar{D}) = \bar{B}$$

$$A(B+\bar{B})CD = ACD$$

$$g = ACD + \bar{B}$$

Minterm notation & NAND-NAND logic

- Any Boolean expression in Minterm notation can be directly realized in NAND-NAND logic.
- Simple (NAND gates only) and fast (only ~~two~~ ²⁻³ gate delay).
- Minimal NAND-NAND expression can be found by K-map.

Example

$$F = \sum m(6, 1, 5) + \sum d(3, 7)$$

Canonical SOP: $F = \overline{A}\overline{B}\overline{C} + A\overline{B}C + A\overline{B}C$

Minimal ~~NAND~~ NAND-NAND expression?

K-map


	BC		AD	
A	0	1	0	1
0	1	1	X	0
1	0	1	X	0

② Minimal SOP: $F = \overline{A}\overline{B} + C$

③ Minimal NAND-NAND: using involution theorem & DeMorgan's

$$F = \overline{\overline{A}\overline{B}} + C \stackrel{\text{DeMorgan}}{=} (\overline{\overline{A}\overline{B}}) \cdot (\overline{\overline{C}})$$

④ Logic diagram:

 

Maxterm notation & NOR-NOR logic

- Any Boolean express in Maxterm notation can be directly realized in NOR-NOR logic.
- Simple and fast.
- Minimal NOR-NOR expression can be found by K-map.

Example

$$F = \prod M(2, 4, 5) + (\prod X M(3, 7))$$

canonical POS: $F = (A + \bar{B} + C) \cdot (\bar{A} + B + C) \cdot (\bar{A} + \bar{B} + C)$

Minimal NOR-NOR:

① K-map


		B	0	0	1	1	0
A	0	1	1	X	0		
1	0	X	1	X	0		

② Minimal POS: $(\bar{A} + C) \cdot (\bar{B})$

③ Minimal NOR-NOR:

$$F = (\bar{A} + C) \cdot (\bar{B}) = \overline{(\bar{A} + C) + (B)}$$

④ Diagram

 

Program Completed

University of Missouri-Rolla

© 2003 Curators of University of Missouri



UNIVERSITY OF MISSOURI-ROLLA
The Name. The Degree. The Difference.