

CpE2210

Introduction to Digital Logic

Dr. Minsu Choi
CH 3. Boolean Algebra & Logic Gates

Date representation & processing

- In the binary # system, information (data) is represented entirely by using the binary digits (bits) 0 and 1.
- Map 0 and 1 to F (false) and T (true) -> logical operations can be done.
- Ex) Logic cell w/ three input ports & one output port.

Basic logic operations

- 1. NOT - changes the value of a variable from 0 to 1 or vice versa.

- Ex) truth table

A	\bar{A}
0	1
1	0

Simplified notation.
called the complement of A.

Another way to represent logic functions. \Rightarrow logic diagrams.

$A \rightarrow \neg \rightarrow \bar{A}$

Graphical symbol of NOT function called an inverter. (operation itself is called inversion)


\Rightarrow buffer. $A \rightarrow \rightarrow A$ Buffer symbol (input = output)

\otimes In your textbook $\bar{A} = A'$ (same meaning different notation).

Continued,

- OR gate

OR gate symbol

 

A	B	$A+B$
0	0	0
0	1	1
1	0	1
1	1	1

OR operation.

($A \text{ OR } B = A+B = A \vee B$)

If one of two inputs is 1, then output is 1.

\Rightarrow OR4 gate. (4-input OR gate)

Continued,


■ AND gate

AND operation ($= A \text{ AND } B = AB = A \wedge B$)

A	B	A · B
0	0	0
0	1	0
1	0	0
1	1	1

→ If both A and B are 1, then 1.

AND gate symbol

 

Basic identities

- Boolean algebra describes the behavior of binary variables that are subjected to the multiple NOT, OR and AND operations. → Some identities can be used to simplify complex logic expressions.

■ NOT identity

$$\overline{(\overline{A})} = A$$

$$\approx \text{NOT} [\text{NOT}(A)] = A$$

) ⇒ involution theorem.

Continued,

- OR identities
$$A + 1 = 1$$
$$A + 0 = A$$
$$A + A = A \rightarrow \text{idempotent theorem}$$
$$A + \bar{A} = 1 \rightarrow \text{complementary property}$$
- AND identities
$$A \cdot 0 = 0$$
$$A \cdot 1 = A$$
$$A \cdot A = A \rightarrow \text{idempotent theorem}$$
$$A \cdot \bar{A} = 0 \rightarrow \text{complementary property}$$

Algebraic laws

- Commutative laws: allows us to arrange variables in any order without changing the result.

$$A + B = B + A$$

$$A \cdot B = B \cdot A$$

Continued,

- Associative laws

$$A + B + C = (A + B) + C = A + (B + C)$$

$$A \cdot B \cdot C = (A \cdot B) \cdot C = A \cdot (B \cdot C)$$

⇒ order of evaluation does not matter.

- Ex) Combination of AND and OR?

$$A \cdot (B + C) \neq A \cdot B + C = (A \cdot B) + C$$

Since AND operation has higher priority.
So, parentheses are necessary.


Continued,

- Distributive laws (both AND and OR)

$$A \cdot (B + C) = (A \cdot B) + (A \cdot C)$$

$$A + (B \cdot C) = (A + B) \cdot (A + C)$$

- Ex) Equivalent logic diagrams

 

output of OR gate
→ input of AND gate

⇒ this kind of wiring scheme is "logic cascade".

NOR and NAND gates

- NOR = NOT-OR, NAND = NOT-AND

$\overline{A+B}$

AB	$\overline{A+B}$
00	1
01	0
10	0
11	0



NOT-OR cascade




NOR gate symbol

inversion bubble.

$\overline{A \cdot B}$

AB	$\overline{A \cdot B}$
00	1
01	1
10	1
11	0

 

AB	$\overline{A+B}$	$\overline{A \cdot B}$
00	1	1
01	0	0
10	0	0
11	0	0

Same!


DeMorgan's Theorems

- Provides alternative expressions that relate the NOR and NAND operations to each other.
- Ex) NOR2 gate with input A & B

$$\overline{A+B} = \overline{A} \cdot \overline{B}$$

⇒ NOR is equivalent to ANDing the complements of the inputs.

$$\text{NOR3: } \overline{A+B+C} = \overline{A} \cdot \overline{B} \cdot \overline{C}$$

 

NAND2

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

$$\overline{A \cdot B \cdot C} = \overline{A} + \overline{B} + \overline{C}$$



AB	$\overline{A \cdot B}$	$\overline{A+B}$
00	1	1
01	1	0
10	1	0
11	0	0

Useful Boolean Identities

$$\textcircled{1} A + AB = A$$

proof) using distributive law.

$$\begin{aligned} A + AB &= A \cdot 1 + A \cdot B \\ &= A(1 + B) \\ &= A \cdot 1 \\ &= A \end{aligned}$$

$$\textcircled{2} A + \bar{A} \cdot B = A + B$$

$$\begin{aligned} \text{proof) } A + \bar{A} \cdot B &= \overline{A + AB} + \bar{A} \cdot B \\ &= A + (A + \bar{A}) \cdot B \\ &= A + 1 \cdot B \end{aligned}$$

$$= A + B$$

Algebraic Reductions

- Reduction of a logic expression to the "simplest" form to implement the function using the smallest # of gates.
- The basic reduction rules are summarized in Table 3.1 (page 70).

$$\begin{aligned} \text{Ex1) } f &= A \cdot B + A \cdot \bar{B} && \downarrow \text{distributive law} \\ &= A(B + \bar{B}) && \downarrow \text{complementary property} \\ &= A \cdot 1 && \downarrow \text{AND identity} \\ &= A \end{aligned}$$

Continued,

■ Ex2)

$$\begin{aligned}
 F &= A \cdot B \cdot C + B \cdot C \Rightarrow B \cdot C \text{ term is common} \\
 &= A \cdot (B \cdot C) + (B \cdot C) \\
 &= (A + 1) \cdot (B \cdot C) \quad \downarrow \text{distributive law} \\
 &= 1 \cdot (B \cdot C) \quad \downarrow \text{OR identity.} \\
 &= B \cdot C \quad \downarrow \text{AND identity.}
 \end{aligned}$$

■ Ex3)

$$\begin{aligned}
 g &= \overline{(a + \bar{b} + c) + (b + \bar{c})} \quad \downarrow \text{DeMorgan's theorem} \\
 &= \overline{(a + \bar{b} + c)} \cdot \overline{(b + \bar{c})} \quad \downarrow \text{once more} \\
 &= (\bar{a} \cdot b \cdot \bar{c}) \cdot (\bar{b} \cdot c) \\
 &= \bar{a} \cdot b \cdot \bar{c} \cdot \bar{b} \cdot c \\
 &= \bar{a} \cdot (b \cdot \bar{b}) \cdot (c \cdot \bar{c}) \\
 &= \bar{a} \cdot 0 \cdot 0 \\
 &= 0. \quad \Rightarrow g \text{ is constant } 0.
 \end{aligned}$$

Continued,

■ Ex4)

$$\begin{aligned}
 h &= (A + B + C) \cdot (A + B) \quad \begin{matrix} \nearrow \text{OR3} \quad \nearrow \text{AND2} \end{matrix} \\
 &= (A + B + C) \cdot A + (A + B + C) \cdot B \quad \downarrow \text{distributive law.} \\
 &= A \cdot A + A \cdot B + A \cdot C + A \cdot B + B \cdot B + B \cdot C \\
 &= A + A \cdot B + B + A \cdot C + B \cdot C \\
 &= A \cdot (1 + B) + B + (A + B) \cdot C \\
 &= (A + B) + (A + B) \cdot C \\
 &= (A + B) \cdot (1 + C) \\
 &= \underline{A + B} \\
 &\quad \downarrow \text{one OR2 gate.}
 \end{aligned}$$

⊗ other logic sets that are equivalent to {NOT, AND, OR} are also complete.

Complete Logic Sets

- A complete logic set of logic operation is one that allows us to create every possible logic functions using only those in the set.

- {NOT, AND, OR} → Any logic function can be implemented by these ops.
- {NOT, OR} → AND can be implemented by DeMorgan's law.

$$\overline{A+B} = A \cdot B$$

Continued,

- {NOT, AND} ex) $\overline{A \cdot B} = A+B$.
- Note that {AND, OR} is not a complete logic set, since NOT cannot be produced by them.
- {NAND}
- {NOR}) are also complete sets.


NAND-based logic

■ Ex) $\overline{A \cdot A} = \bar{A} \rightarrow \text{NOT}$

$\overline{A \cdot B} = A + B \rightarrow \text{OR}$

ex) $f = x + \bar{y} = \overline{\overline{x + \bar{y}}} = \overline{\bar{x} \cdot y}$

involution theorem.

 

NAND gates only.


NOR-based logic

$\overline{A + A} = \bar{A} \text{ (NOT)}$

$\overline{A + B} = \bar{A} \cdot \bar{B} \text{ (AND)}$

■ Ex) $g = a \cdot b + c$
 $= \overline{\overline{a \cdot b + c}} = \overline{(\bar{a} \cdot \bar{b}) \cdot \bar{c}} = \overline{(\bar{a} + \bar{b}) \cdot \bar{c}}$
 $= \overline{(\bar{a} + \bar{b})} + c = \overline{\bar{a} + \bar{b}} + c$

De Morgan's reduction



 


NOR only.

⊗ Shape-specific symbols have been introduced
so far

IEEE Logic Gate Symbols

   - Very common in practice (alternative way).
- IEEE is an acronym that stands for the Institute of Electrical & Electronics Engineers, a professional organization for electrical engineers.



Continued,

Program Completed

University of Missouri-Rolla

© 2003 Curators of University of Missouri



UNIVERSITY OF MISSOURI-ROLLA
The Name. The Degree. The Difference.